

Course Name:	Digital Design Laboratory	Semester:	III
Date of Performance:	24 / 07 / 2023	Batch No:	B-2
Faculty Name:		Roll No:	16010122151
Faculty Sign & Date:		Grade/Marks:	___/25

Experiment No: 2
Title: Binary Adders and Subtractors

Aim and Objective of the Experiment:
To implement half and full adder-subtractor using gates and IC 7483

COs to be achieved:
CO2: Use different minimization technique and solve combinational circuits.

Tools used:
Trainer kits

Theory:

Adder: The addition of two binary digits is the most basic operation performed by the digital computer. There are two types of adder:

- Half adder
- Full adder

Half Adder: Half adder is a combinational logic circuit with two inputs and two outputs. It is the basic building block for the addition of two single-bit numbers.

Full adder: A half adder has a provision not to add a carry coming from the lower order bits when multi-bit addition is performed. for this purpose, a third input terminal is added and this circuit is to add A, B, and C where A and B are the nth order bits of the number A and B respectively and C is the carry generated from the addition of (n-1) order bits. This circuit is referred to as full adder.

Subtractor: Subtraction of two binary digits is one of the most basic operations performed by digital computer. there are two types of subtractors:

- Half subtractor

- Full subtractor

Half subtractor: Logic circuit for the subtraction of B from A where A,B are 1 bit numbers is referred to as half subtract or .the subtract or process has two input and difference and borrow are the two outputs.

Full subtractor: As in the case of the addition using logic gates, a full subtractor is made by combining two half-sub tractors and an additional OR-gate. A full subtractor has the borrow in capability (denoted as BOR_{IN}) and so allows cascading which results in the possibility of multi-bit subtraction.

IC 7483

For subtraction of one binary number from another, we do so by adding 2's complement of the former to the latter number using a full adder circuit.

IC 7483 is a 16 pin, 4-bit full adder. This IC has a provision to add the carry output to transfer and end around carry output using Co and C4 respectively.


2's complement: 2's complement of any binary no. can be obtained by adding 1 in 1's complement of that no. e.g. 2's complement of $+(10)_{10} = 1010$ is

$$\begin{array}{r}
 \text{1C of } 1010 \qquad 0101 \\
 \qquad \qquad \qquad + \quad 1 \\
 \hline
 -(10)_{10} \qquad \qquad 0110
 \end{array}$$

In 2's complement subtraction using IC 7483, we are representing negative number in 2's complement form and then adding it with 1st number.


Implementation Details:

Half Adder Block Diagram

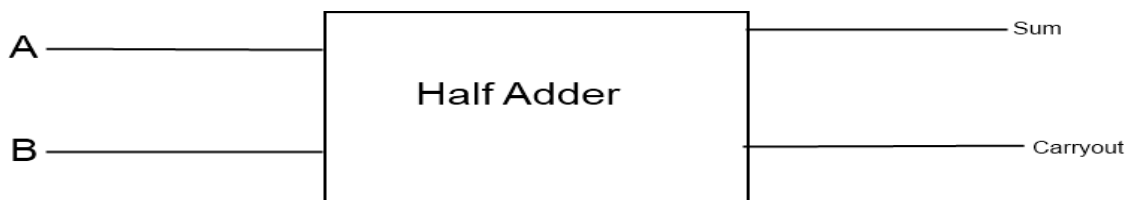

Block Diagram of Half Adder

Half Adder Circuit

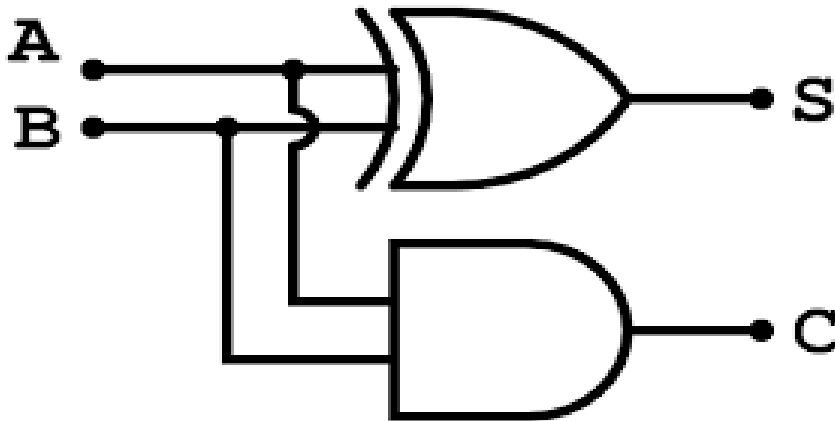

Truth Table for Half Adder

Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


From the truth table (with steps):

$$S = AB' + A'B$$


$$C = A.B$$

Inputs				Outputs	
A	B	$A \oplus B$	$A \cdot B$	S	C
0	0	0	0	0	0
0	1	1	0	1	0
1	0	1	0	1	0
1	1	0	1	0	1

Full Adder Block Diagram

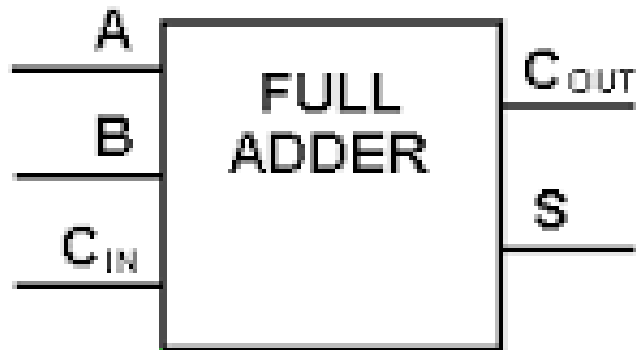

Full Adder Circuit

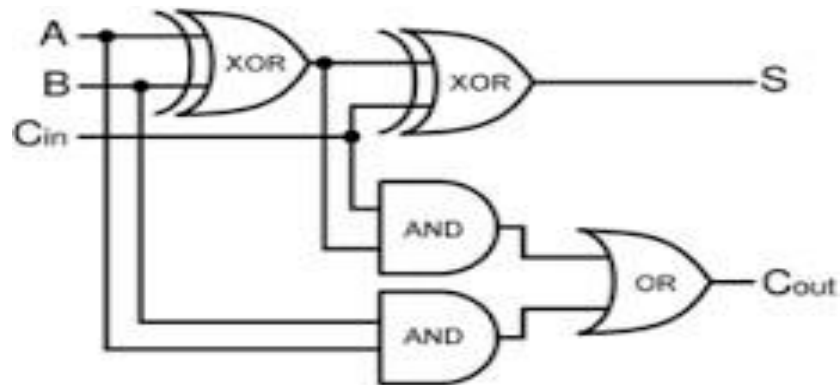

Truth Table for Full Adder

Sr. No	A	B	Cin	S	Cout
1.	0	0	0	0	0
2.	0	0	1	1	0
3.	0	1	0	1	0
4.	0	1	1	0	1
5.	1	0	0	1	0
6.	1	0	1	0	1
7.	1	1	0	0	1
8.	1	1	1	1	1


From the truth table (with steps):

$$S = A'B'Cin + A'BCin' + AB'Cin' + ABCin$$


$$Cout = ACin + AB + BCin$$

Inputs			Operations					Ouputs	
A	B	Cin	$A \oplus B = D$	$D \oplus Cin = E$	$D \cdot Cin = F$	$A \cdot B = G$	$F + G = H$	S	C
0	0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	1	0
0	1	0	1	1	0	0	0	1	0
0	1	1	1	0	1	0	1	0	1
1	0	0	1	1	0	0	0	1	0
1	0	1	1	1	1	0	1	0	1
1	1	0	0	0	0	1	1	0	1
1	1	1	0	1	0	1	1	1	1

Half Subtractor Block Diagram

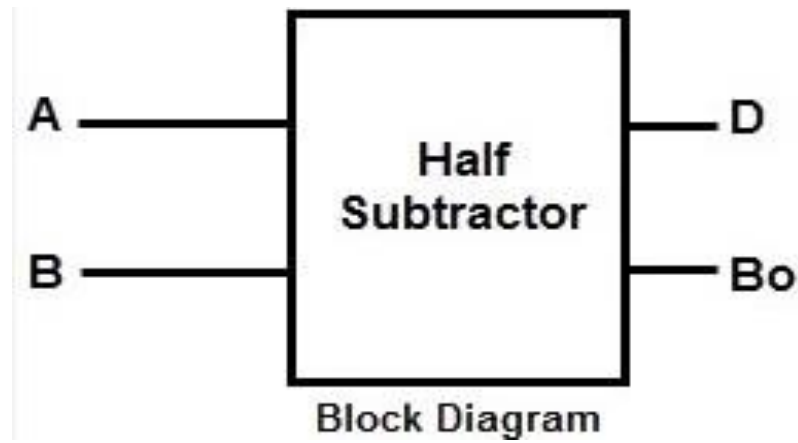

Half Subtractor Circuit

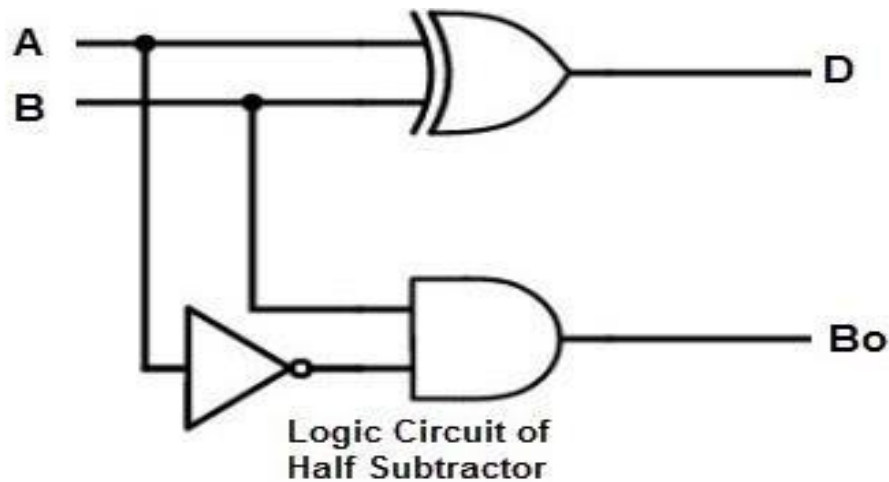

Truth Table for Half Subtractor

A	B	DIFFERENCE(D)	BORROW(Bo)
0	0	0	0
1	0	1	0
0	1	1	1
1	1	0	0

From the truth table (with steps) :

$$\text{Difference (D)} = A'B + AB'$$


$$\text{Borrow(B)} = A'B$$

Inputs					Outputs	
A	B	$\sim A = C$	$A \oplus B = E$	$B \cdot C = F$	D	Borrow
0	0	1	0	0	0	0
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	1	0	0	0	0	0

Full Subtractor Block Diagram



Full Subtractor Circuit

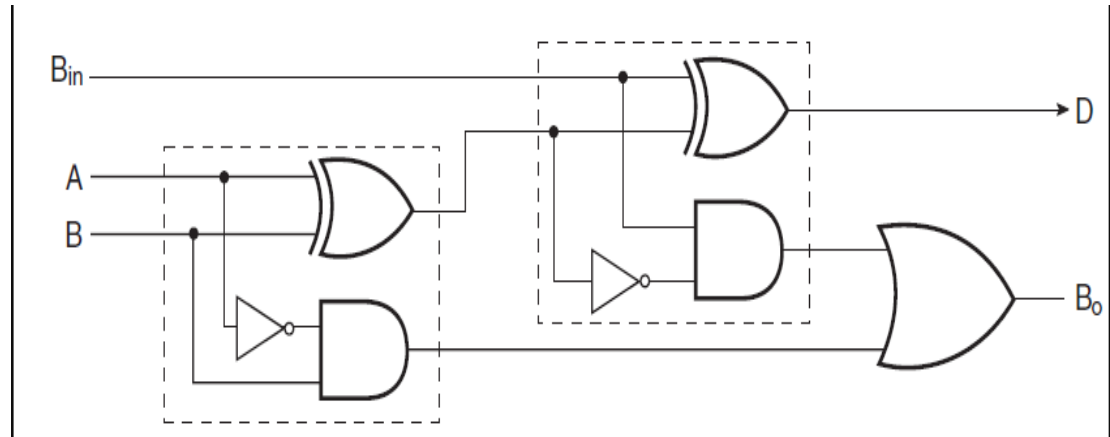

Truth Table for Full subtractor

A	B	BIN	D	BOROUT
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

From the truth table (with steps):

$$\text{Difference} = A'B'Bin + A'BBin' + AB'Bin' + ABBin$$

$$\text{Borrow out} = A'B + A'Bin + BBin$$

Input										Output	
A	B	Bin	$A \oplus B =$ C	$\sim A = E$	$E.B = F$	$Bin \oplus C$ = G	$\sim C = F$	$F.Bin =$ H	$F + H = I$	D	Borr _{out}
0	0	0	0	1	0	0	1	0	1	0	0
0	0	1	0	1	0	1	1	1	1	1	1
0	1	0	1	1	1	1	0	0	0	1	1
0	1	1	1	1	1	0	0	0	0	0	1
1	0	0	1	0	0	1	0	0	0	1	0
1	0	1	1	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	1	0	0
1	1	1	0	0	0	1	1	1	1	1	1

Example:

1) $7_{10} - 2_{10} = 5_{10}$

7 0111

2 0010

1'C of 2

1101


+ 1

2'C of 2


1110

0111 + 1110 1 0101


Pin Diagram IC7483

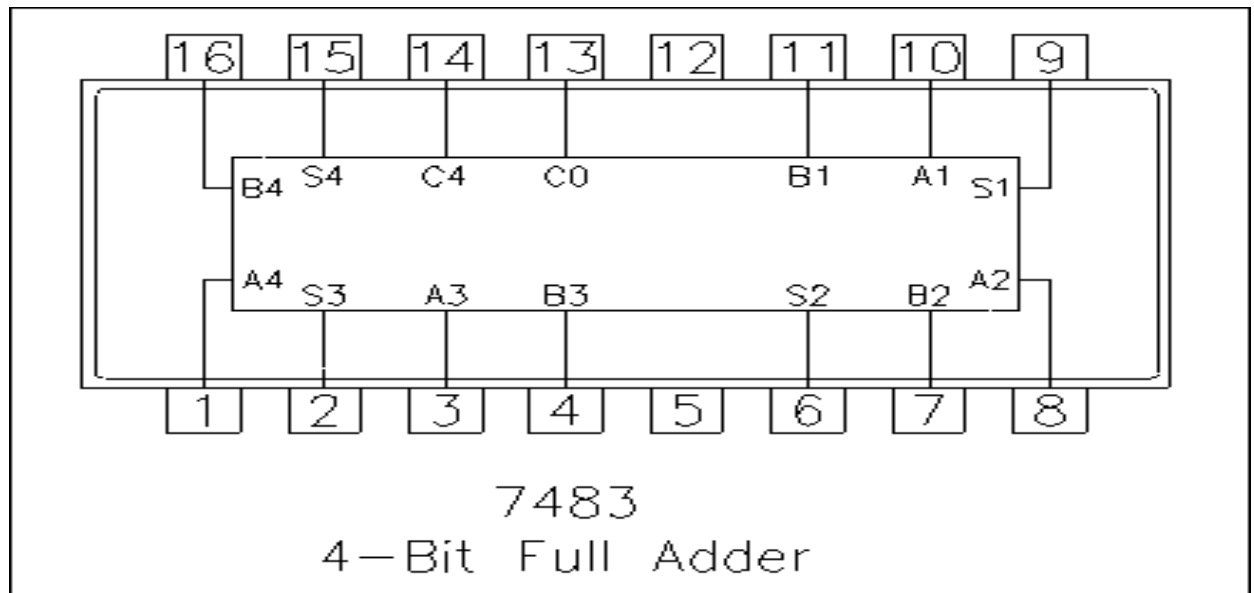

Adder

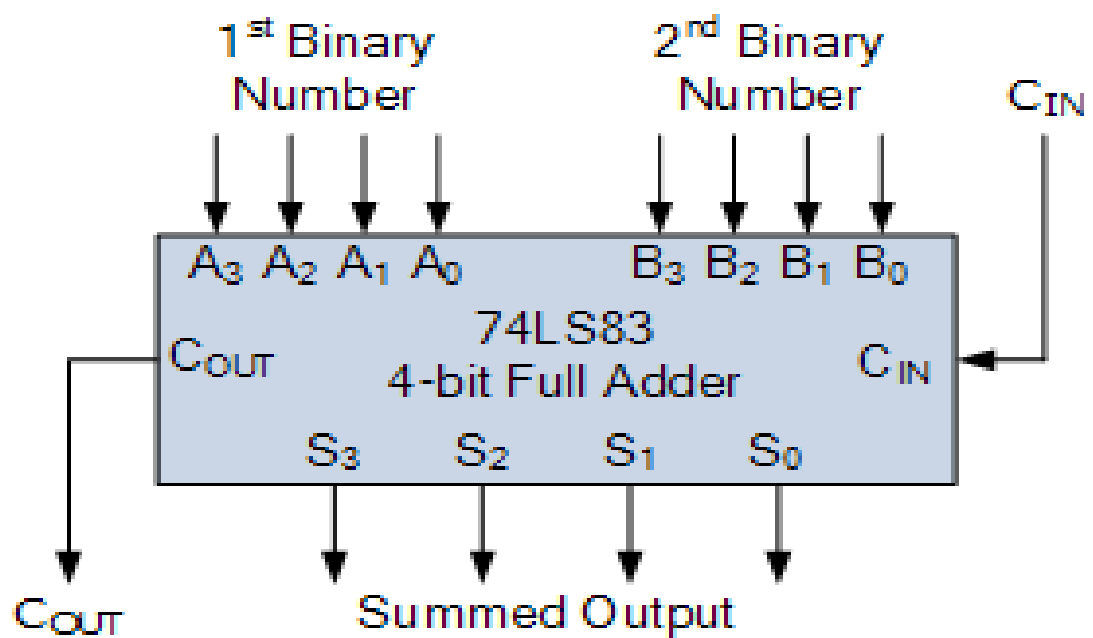

Subtractor

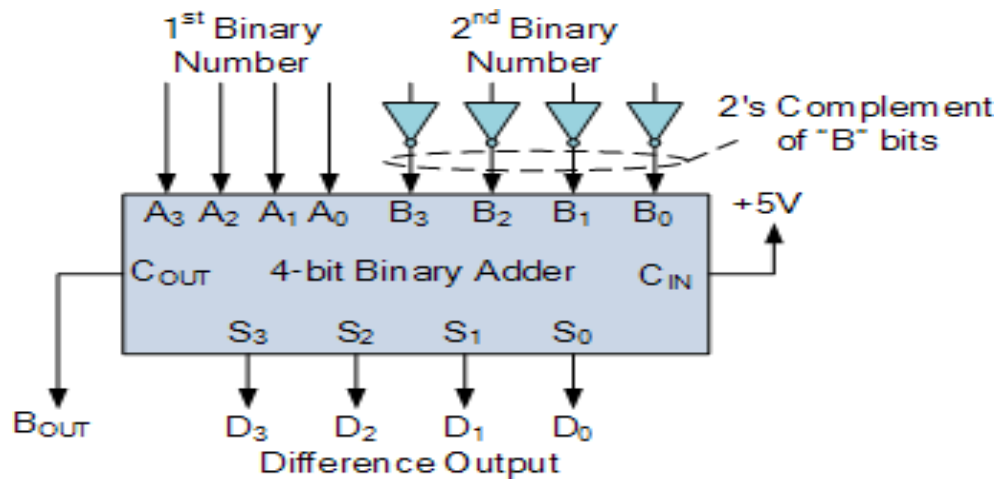


Implementation Details

Procedure:

- 1) Locate the IC 7483 and 4-not gates block on trainer kit.
- 2) Connect 1st input no. to A4-A1 input slot and 2nd (negative) no. to B4-B1 through 4-not gates (1C of 2nd no.)
- 3) Connect high input to Co so that it will get added with 1C of 2nd no. to get 2C.
- 4) Connect 4-bit output to the output indicators.
- 5) Switch ON the power supply and monitor the output for various input combinations.


Post Lab Subjective/Objective type Questions:

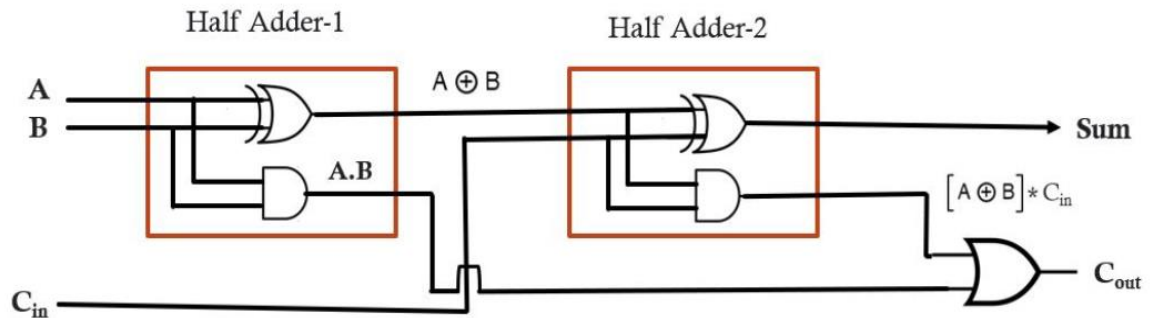1. Design a full adder using two half adders.



1. Perform the following Binary subtraction with the help of appropriate ICs:
 - a. 6-4

SWARUP.

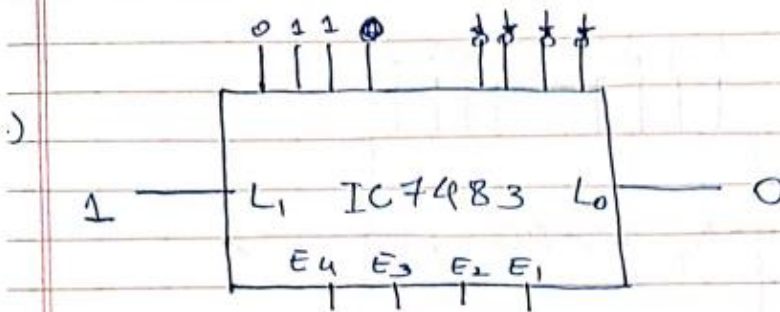

$$6 - 4$$

$$(6)_{10} = (0110)_2$$

$$(4)_{10} = (0100)_2$$

Now 2's complement of 4 gives us 4

1's complement of 4

$$4 = 0100$$

$$1's \text{ complement} = 1011$$

For 2's complement:

$$\begin{array}{r} 1011 \\ + \quad 1 \\ \hline 1100 \end{array}$$

-4 gives 1011

$$6 - 4 \Rightarrow 6 + (-4)$$

$$= 0110$$


$$1000$$

$$0010$$

$$\Rightarrow (2)_{10}$$

classmate
Date _____
Page _____

(b) 5 - 8

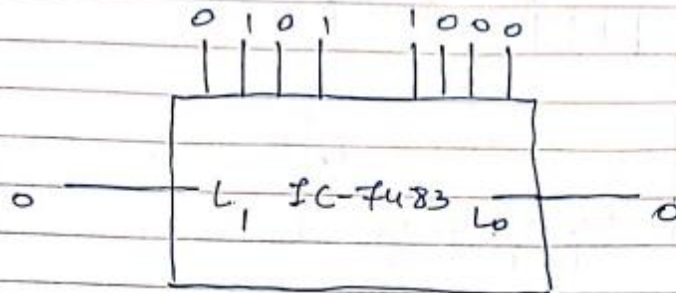

$$(5)_{10} = (0101)_2$$

$$(8)_{10} = (1000)_2$$

$$5 - 8 \Rightarrow 5 + (-8)$$

$$1's \text{ of } 8 \Rightarrow 0111$$

$$2's \text{ of } 8 \Rightarrow \begin{array}{r} 0111 \\ + 1 \\ \hline 1000 \end{array}$$

$$5 + (-8) \Rightarrow 0101$$

$$\begin{array}{r} 1000 \\ 0101 \\ \hline 01101 \end{array}$$

\therefore Number is negative

$$1's \text{ Complement} \Rightarrow 10010$$

$$2's \text{ complement} \Rightarrow 10010$$

$$\text{Carry} \leftarrow 10011$$

$$\Rightarrow (0011)_2 = (3)_{10}$$

$$\therefore 5 - 8 = \underline{\underline{-3}}$$

(c) $7 - 9$

$$(7)_{10} = (0111)_2$$

$$(9)_{10} = (1001)_2$$

$$7 - 9 = 7 + (-9)$$

$$1's \text{ complement of } 9 \Rightarrow 0110$$

$$2's \text{ complement of } 9 \Rightarrow 0110$$

$$\begin{array}{r} 0110 \\ + 1 \\ \hline 0111 \end{array}$$

$$\begin{array}{r} 7 + (-9) \Rightarrow 0111 \\ + 0111 \\ \hline 0110 \end{array}$$

\therefore No is negative

$$1's \Rightarrow 10001$$

$$2's \text{ complement} \Rightarrow 10001$$

$$\begin{array}{r} 10001 \\ \leftarrow \text{Carry} \end{array}$$

$$\therefore (0010)_2 = (2)_{10}$$

$$\therefore \underline{7 - 9 = -2}$$

Conclusion:

Circuits of binary adder and sub tractors were studied on the IC kit using Connectors and tested using sample values.

Signature of faculty in-charge with Date: