

<b>Course Name:</b>	<b>Digital Design Laboratory</b>	<b>Semester:</b>	<b>III</b>
<b>Date of Performance:</b>	<b>5/ 10/ 2023</b>	<b>Batch No:</b>	<b>B-2</b>
<b>Faculty Name:</b>		<b>Roll No:</b>	<b>16010122151</b>
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	<b>___/25</b>

## **Experiment No: 7** **Title: Asynchronous Counter**

### **Aim and Objective of the Experiment:**

To design and implement 3 bit Asynchronous up counter using JK Flip Flop

### **COs to be achieved:**

**CO3:** Design synchronous and asynchronous sequential circuits.


### **Tools used:**


Trainer kits

### **Theory:**

**Circuit diagram of 3 bit Asynchronous Up counter using JK FF (IC 7476)**

**Logic Diagram for 3- bit Up Counter:**

 

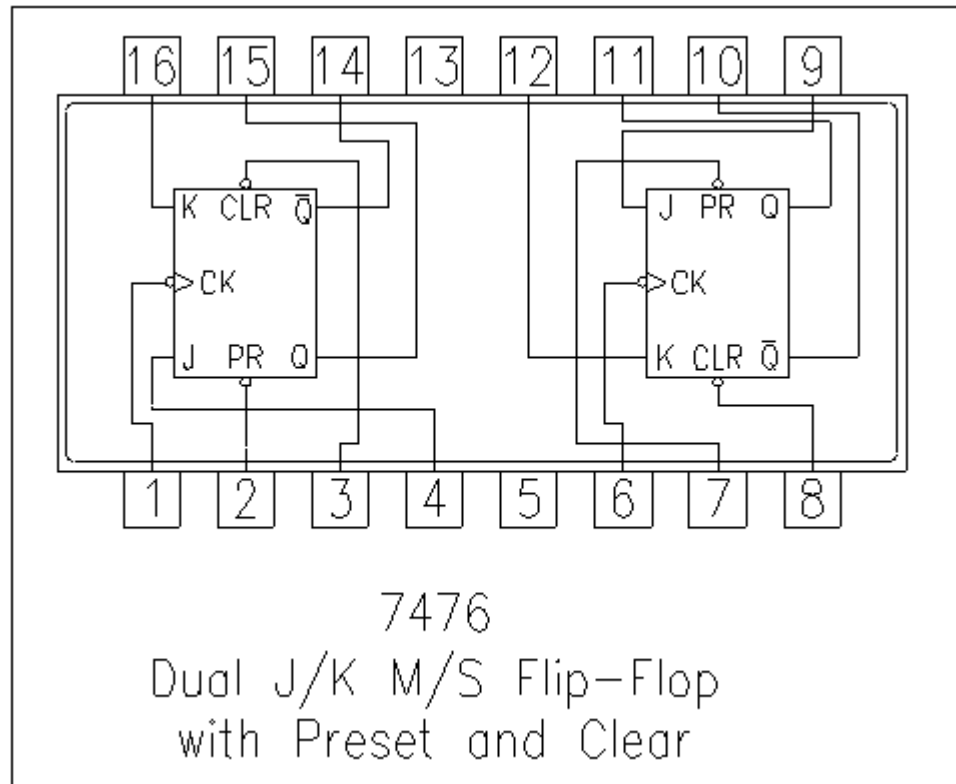**Pin diagram of JK FF (IC 7476)**

**Implementation Details**
**Procedure**

- 1) Locate IC 7476 JK FF on Digital trainer kit
- 2) Apply various inputs to appropriate pins as per the circuit diagram of the 3 bit Asynchronous up counter with reference to the pin configuration of the IC.
- 3) Make sure of Reset and Clear Pins connections with reference to data sheet information.
- 4) Connect a pulsar switch to the clock input.
- 5) Verify the working and prepare a truth table.

**Post Lab Subjective/Objective type Questions:**
**1. How JK FF need to be configured to use for counter operation?**

To configure a JK flip-flop for use in a counter operation, you typically connect multiple JK flip-flops in a cascade (also known as a ripple counter) and connect their J and K inputs appropriately. In a simple up-counter, you connect the J and K inputs of each JK flip-flop as follows:

The J input of the first flip-flop is set to 1, and the K input is set to 0.

The J input of each subsequent flip-flop is connected to the Q output of the previous flip-flop.

The K input of each subsequent flip-flop is also connected to the Q output of the previous flip-flop, but through an inverter (NOT gate).

**2. What changes are required to use the same counter as 3 bit asynchronous down counter?**

To use the same counter as a 3-bit asynchronous down counter, you need to modify the connections as follows:

- The J input of the first flip-flop remains set to 1, and the K input is set to 0.
- The J and K inputs of each subsequent flip-flop are connected to the complement (opposite) of the Q output of the previous flip-flop.

**3. Draw the timing diagram of 3 bit Asynchronous up counter**

Clock: 

Bit 0: 0 1 0 1 0 1 0 1

Bit 1: 0 0 1 1 0 0 1 1

Bit 2: 0 0 0 0 1 1 1 1

Each bit changes state on the rising edge of the clock signal, resulting in an increment by 1 for each clock cycle.

**4. What is mod n concept used in counters?**

The "mod n" concept in counters refers to the counting range of the counter. A counter can count from 0 to (n-1) before it resets to 0. For example, in a mod-5 counter, the counter will count from 0 to 4 and then reset to 0, effectively having 5 unique states. The modulo value (n) determines the counting range, and it's also the number of different states the counter can represent.

**5. For Mod-5 counter how many JK FFs are required?**

For a Mod-5 counter, you would need three JK flip-flops. This is because a 3-bit counter can represent values from 0 to 7 ( $2^3 = 8$ ), but for a Mod-5 counter, you only need to count from 0 to 4. Therefore, a 3-bit counter can be used, and it will require three JK flip-flops to represent these 5 states.

**Conclusion:**

The experiment effectively demonstrated the configuration, operation, and practical implementation of a 3-bit asynchronous up counter using JK flip-flops, providing valuable insights into digital counter circuits and their applications.

**Signature of faculty in-charge with Date:**