

<b>Course Name:</b>	<b>Digital Design Laboratory</b>	<b>Semester:</b>	<b>III</b>
<b>Date of Performance:</b>	<u>  21  </u> / <u> 08 </u> / <u> 23 </u>	<b>Batch No:</b>	<b>B-2</b>
<b>Faculty Name:</b>		<b>Roll No:</b>	<b>16010122151</b>
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	<u>      </u> /25

**Experiment No: 4**  
**Title: 4-bit magnitude comparator**

**Aim and Objective of the Experiment:**

To design and implement 1-bit comparator using logic gates and verify 4-bit magnitude comparator using IC 7485

**COs to be achieved:**


**CO2:** Use different minimization techniques and solve combinational circuits.

**Tools used:**

Trainer kits

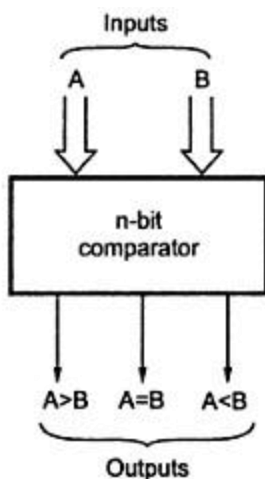**Theory:**

**Comparator:** The comparison of two numbers is an operator that determines one number is greater than, less than (or) equal to the other number. A magnitude comparator is a combinational circuit that compares two numbers A and B and determines their relative magnitude. The outcome of the comparator is specified by three binary variables that indicate whether  $A > B$ ,  $A = B$  (or)  $A < B$ .



### 1-bit Comparator Implementation Details:

#### Truth Table

Input		Output		
A	B	$Y_{A=B}$	$Y_{A>B}$	$Y_{A<B}$
0	0	1	0	0
0	1	0	0	1
1	1	0	1	0
1	0	0	0	1


#### From the Truth Table:

$$(A<B) = A'B$$

$$(A=B) = A'B' + AB$$


$$(A>B) = AB'$$

#### Logic Diagram of 1-bit Comparator

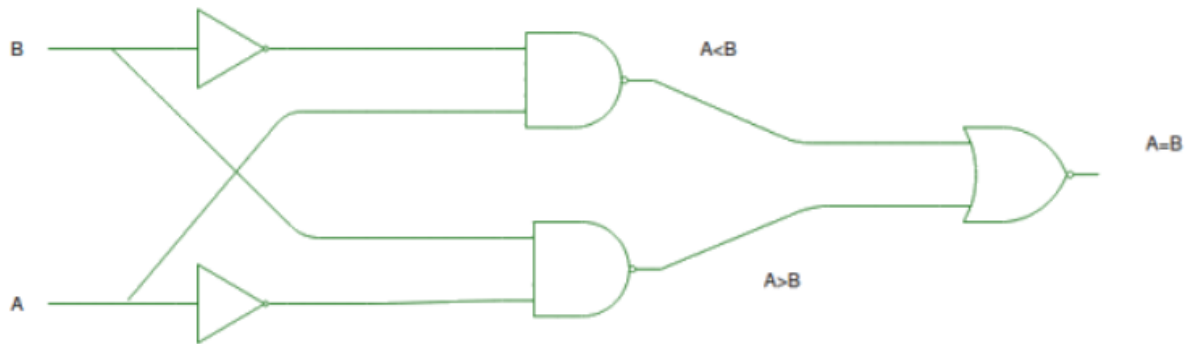


## Four Bit Magnitude Comparator Implementation Details

### Pin Diagram of IC 7485

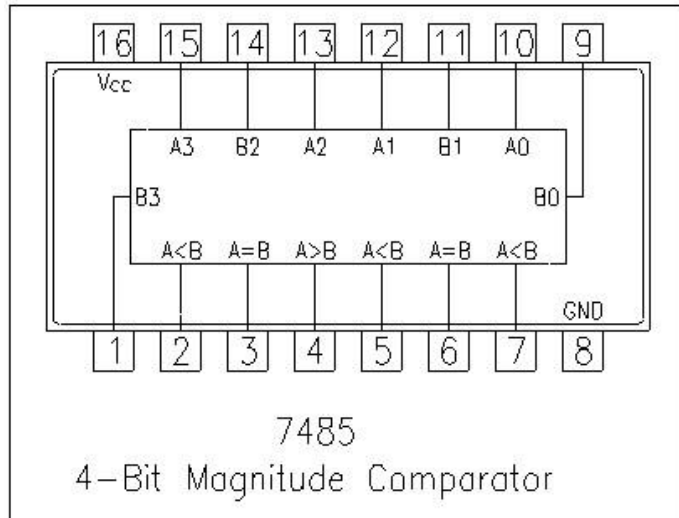

### Logic Diagram of IC 7485

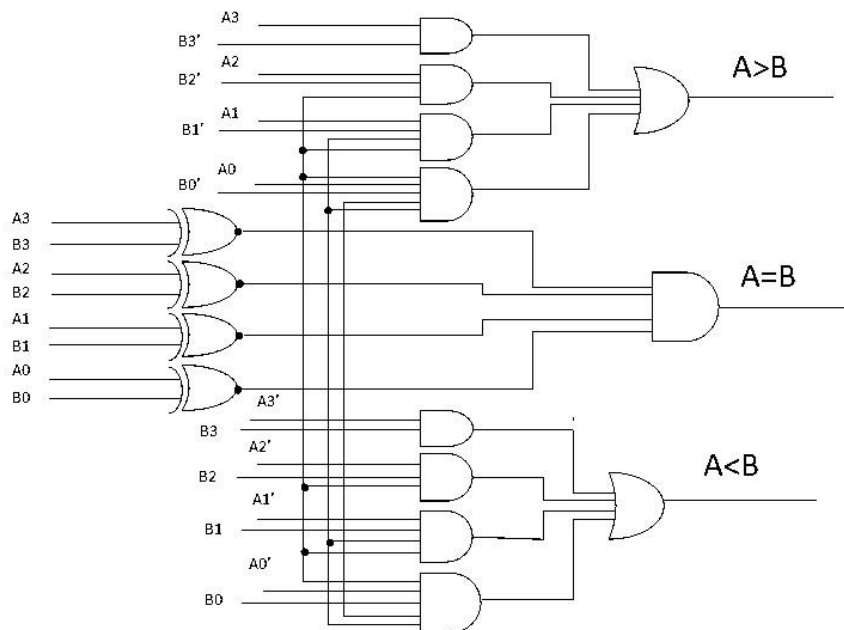

### Comparing Table

INPUTS of 4 bit Comparator				OUTPUT		
$A_3, B_3$	$A_2, B_2$	$A_3, B_3$	$A_2, B_2$	$A_3, B_3$	$A_2, B_2$	$A_3, B_3$
$A_3 > B_3$	X	X	X	H	L	L
$A_3 < B_3$	X	X	X	L	H	L
$A_3 = B_3$	$A_2 > B_2$	X	X	H	L	L
$A_3 = B_3$	$A_2 < B_2$	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$	X	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	L	H

Where H = High Output, L = Low Output, X = Don't Care

### Implementation Details

#### Procedure:

- 1) Locate the IC 7485 on the trainer kit.
- 2) Connect 1<sup>st</sup> input no. to A3-A0 input slot and 2<sup>nd</sup> to B3-B0.
- 3) Connect the output  $Y_{A>B}$ ,  $Y_{A<B}$  and  $Y_{A=B}$  to the output indicators.
- 4) Switch ON the power supply and monitor the output for various input combinations.

**Post Lab Subjective/Objective type Questions:**

1. Design 2-bit magnitude comparator.

A <sub>1</sub>	A <sub>0</sub>	B <sub>1</sub>	B <sub>0</sub>	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0


**From the Truth Table:**

$$(A < B) = A_1'B_1 + A_0'B_1B_0 + A_1'A_0'B_0$$


$$(A = B) = A_1'A_0'B_1'B_0' + A_1'A_0B_1'B_0 + A_1A_0B_1B_0 + A_1A_0'B_1B_0'$$

$$(A > B) = A_1B_1' + A_0B_1'B_0' + A_1A_0B_0'$$

**Logic Diagram:**

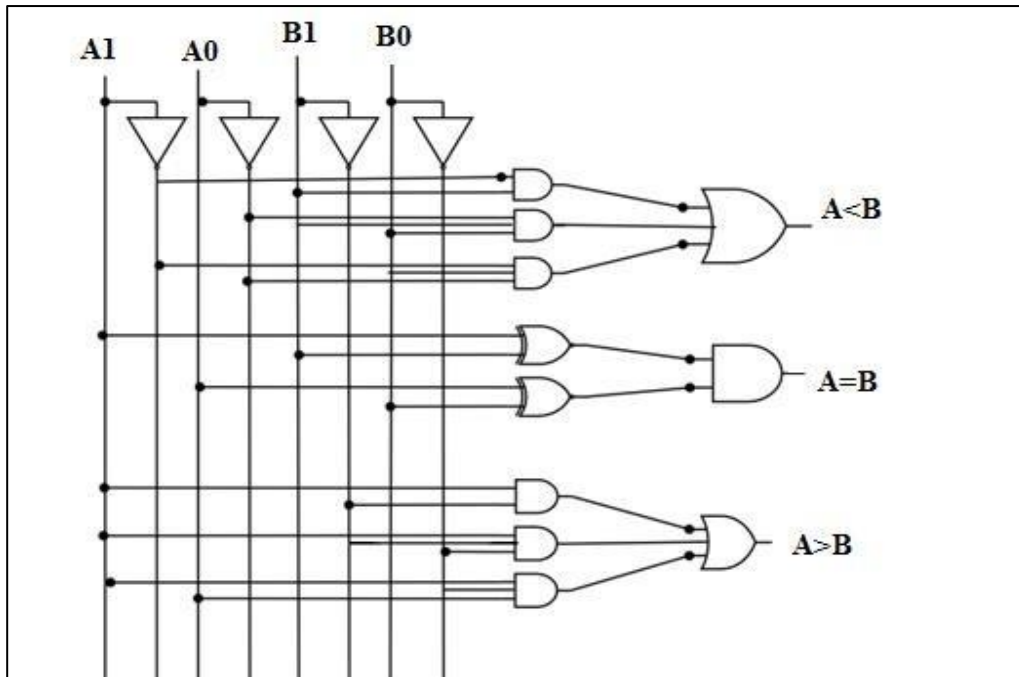

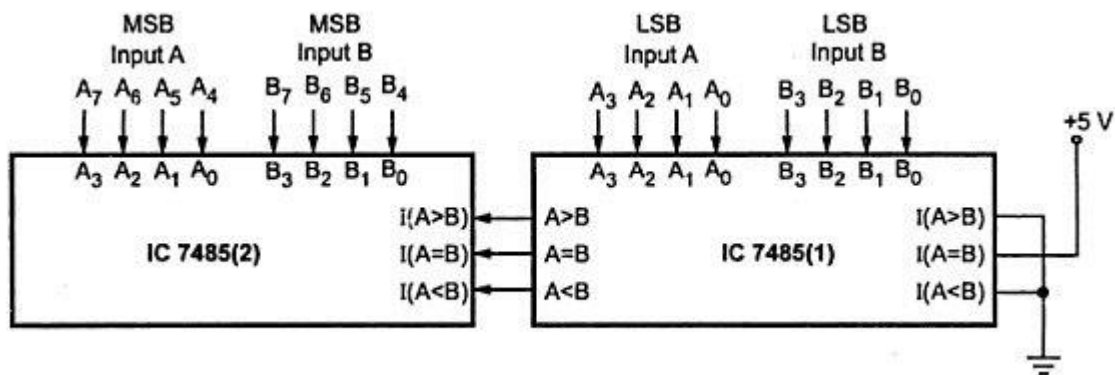2. How can we implement 5-bit magnitude comparator using IC 7485.



**Conclusion:**

From this experiment we learnt the concept of comparators .



**SOMAIYA**  
VIDYAVIHAR UNIVERSITY

K J Somaiya College of Engineering

**K. J. Somaiya College of Engineering, Mumbai-77**

(A Constituent College of Somaiya Vidyavihar University)

**Department of Computer Engineering**



**Signature of faculty in-charge with Date:**